

FAMU - FSU College of Engineering
Department of Electrical and Computer Engineering Spring
2021 Semester
EEL 4905L - FPLDs Lab Report

Section No: 3

Lab Instructor: Rajesh Thomas

Lab No: Project

Lab Title: FIR Filters

Name: Marc Abad

Date Performed: 4/7/21

Date Delivered: 4/9/21

Contents

1	Introduction.....	3
2	Requirements	3
3	Theoretical Design	3
3.1	Design Narrative	3
3.2	Top-level design.....	4
4	Simulation Results.....	5
5	Optimization Results	7
6	Discussion	7
7	Summary and Lessons Learned	8
8	Appendix 1.....	8
9	Appendix 2.....	9
10	Appendix 3.....	10
11	Appendix 4.....	11
12	Appendix 5.....	12

1 Introduction

The purpose of this lab is to introduce students to direct and transpose forms of Finite Impulse Response (FIR) Digital Filters. Main objectives of this lab are to develop a direct form FIR filter, a transpose FIR filter, a transpose FIR filter with pipelining, and to compare balance, performance, power, and area optimizations.

2 Requirements

Inputs:

Name	Description
rst	Input clock that drives the simulation.
clk	Reset input to reset internal signals
x	Discrete input at current time

Local:

Name	Description
Shift_reg	Signal of shifted input x
prod	Signal of products of coefficients and input
sum	Signal of sums of products

Outputs:

Name	Description
y	Discrete output at current time

3 Theoretical Design

3.1 Design Narrative

This design is a finite impulse response digital filter. It is designed to implement the following equation.

$$y(n) = \sum_{k=0}^{N-1} h(n)x(n-k)$$

This lab uses both the direct form and transpose form of the FIR filter. Both forms are created by continually adding products. The following figures represent the networks

of the direct and transpose form.

 


Figure 1. Direct Form Realization of an FIR System


 


Figure 2. Transposition of the network of Figure 1

3.2 Top-level design

 

rst – Input signal that will reset all internal signals to 0 and restart the main filter process (shift_reg, prod, sum).

clk - Input signal with period of 20 ns that will either assign shift_reg or sum on rising edge.

x – Input std_logic_vector that is multiplied by filter coefficients in the multipliers.

shift_reg – Signed array equal to the shifted signed value of x


prod – Signed array equal to either the product of coefficients and shift_reg for direct form, or coefficients and x for transpose form.

sum – Signed array that adds the current and previous products.


y – Output std_logic_vector equal to the final sum value (NUM_COEF-1 for direct, 1 for transpose).

4 Simulation Results


Appendix 1 Simulation Results

 




Appendix 3 Simulation Results

 

Appendix 4 Simulation Results

 

   Appendix 5 Simulation Results (Low-pass, equiripple FIR filters)



5 Optimization Results

Direct Form FIR Filter

Optimization	Logic Utilization (ALM)	Multipliers	Fmax (MHz)	Power (mW)
Balanced	47	119	494.56	354.39
Performance	47	119	574.05	354.39
Power	47	119	572.41	354.39
Area	47	119	557.41	354.39

Transpose Form FIR Filter

Optimization	Logic Utilization (ALM)	Multipliers	Fmax (MHz)	Power (mW)
Balanced	56	119	334	354.33
Performance	56	119	335.8	354.33
Power	56	119	346.5	354.33
Area	57	119	344	354.33


Transpose Form Pipelined FIR Filter

Optimization	Logic Utilization (ALM)	Multipliers	Fmax (MHz)	Power (mW)
Balanced	56	119	304.32	354.39
Performance	56	119	289.94	354.39
Power	56	119	308.07	354.39
Area	56	119	344.35	354.39

6 Discussion

- 1) A direct form FIR filter was implemented in Appendix 1 and verified via simulation.
- 2) A transpose form FIR filter without pipelining was implemented in Appendix 3. This was done by converting the affected ranges from (0 TO NUM_COEF-1) to (NUMCOEF DOWNT0 1). This was done in order to follow the transposition figure provided in the Lab Manual (displayed above in 3.1 Design Narrative). An additional change not already implemented would be calculating sum (0 TO NUM_COEF-2) and manually calculating the y output to be sum(2) + prod(1). This would eliminate an extra resistor in the RTL Viewer. This design was verified via simulation.

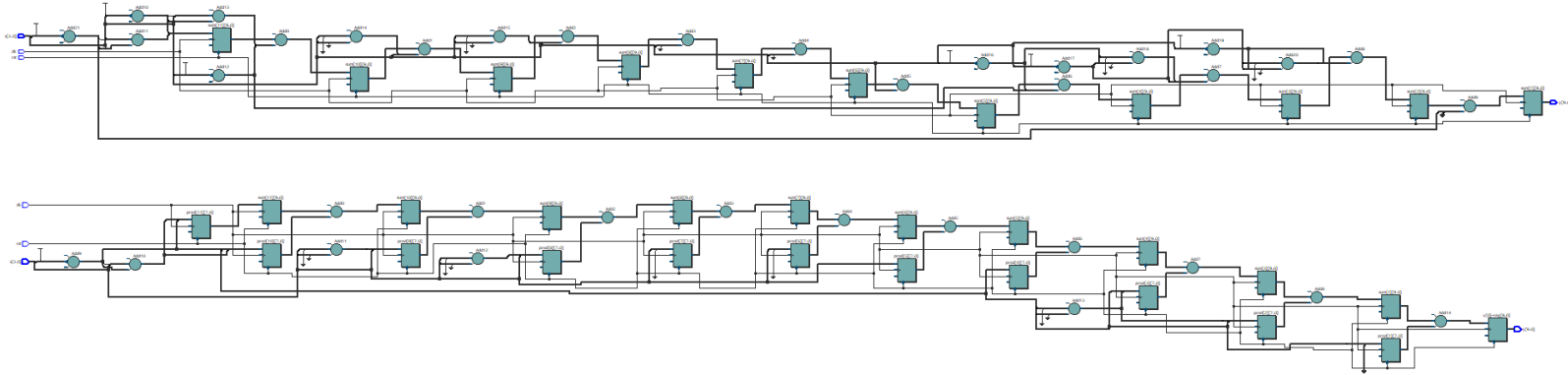- 3) A transpose form FIR filter with pipelining was implemented in Appendix 4. This was done by moving the multiplier and y output statements to the positive edge of the process. This design was verified via simulation. This design also changed the RTL view below and lowered the Fmax overall.



- 4) The direct form optimizations all utilized 47 ALMs. The transpose form filters all utilized 56 ALMs, except for Area using 1 more at times. All of the filter optimizations utilized 119 multipliers. Balanced optimization had the lowest Fmax, except for the pipelined filter. Performance optimization had the highest Fmax with the direct form filter. Power optimization had the highest Fmax with the transpose form unpipelined filter. Area optimization had the highest Fmax with the transpose form pipelined filter. Estimated power consumption was mostly constant with less used in the transpose form unpipelined filter.

7 Summary and Lessons Learned

In conclusion, the direct form FIR filter, the transpose form FIR filter, and the transpose form pipeline FIR filter were successfully created, tested, and verified through simulation.

One lesson I learned was to create my DO file first and simulate my code while making changes so I can find mistakes faster.

8 Appendix 1

VHDL Code for Direct Form FIR Digital Filter (provided from lab manual)


```

2  LIBRARY ieee;
3  USE ieee.std_logic_1164.ALL;
4  USE ieee.numeric_std.ALL;
5
6  ENTITY fir_direct IS
7  GENERIC (
8      NUM_COEF : NATURAL := 11;
9      BITS_COEF : NATURAL := 4;
10     BITS_IN : NATURAL := 4;
11     BITS_OUT : NATURAL := 10);
12  PORT (
13     clk, rst : IN STD_LOGIC;
14     x : IN STD_LOGIC_VECTOR(BITS_IN-1 DOWNTO 0);
15     y : OUT STD_LOGIC_VECTOR(BITS_OUT-1 DOWNTO 0));
16  END ENTITY;
17
18  ARCHITECTURE fpga OF fir_direct IS
19     TYPE int_array IS ARRAY (0 TO NUM_COEF-1) OF INTEGER RANGE
20         -2**(BITS_COEF-1) TO 2**(BITS_COEF-1)-1;
21     CONSTANT coef : int_array := (-8,-5,-5,-1,1,2,2,3,5,7,7);
22     TYPE signed_array IS ARRAY (NATURAL RANGE <>) OF SIGNED;
23     SIGNAL shift_reg : signed_array(0 TO NUM_COEF-1)(BITS_COEF-1 DOWNTO 0);
24     SIGNAL prod: signed_array(0 TO NUM_COEF-1)(BITS_IN+BITS_COEF-1 DOWNTO 0);
25     SIGNAL sum: signed_array(0 TO NUM_COEF-1)(BITS_OUT-1 DOWNTO 0);
26  BEGIN
27     PROCESS(clk,rst)
28     BEGIN
29         IF rst = '0' THEN
30             shift_reg <= (OTHERS => (OTHERS => '0'));
31         ELSIF rising_edge(clk) THEN
32             shift_reg <= SIGNED(x) & shift_reg(0 TO NUM_COEF-2);
33         END IF;
34     END PROCESS;
35
36     mult: FOR i IN 0 TO NUM_COEF-1 GENERATE
37         prod(i) <= TO_SIGNED(coef(i),BITS_COEF) * shift_reg(i);
38     END GENERATE;
39
40     sum(0) <= resize(prod(0),BITS_OUT);
41     adder: FOR i IN 1 TO NUM_COEF-1 GENERATE
42         sum(i) <= sum(i-1) + prod(i);
43     END GENERATE;
44
45     y <= STD_LOGIC_VECTOR(sum(NUM_COEF-1));
46  END ARCHITECTURE;

```

9 Appendix 2

DO Code for ModelSim simulation

```
1  ##### Compile design
2  vlib work
3  #vcom -93 lab8d.vhd
4  vcom -2008 fir_direct.vhd
5  vsim work.fir_direct(fpga)
6
7  ##### Add I/O signals to wave window
8  radix decimal
9  add wave -divider "Marc Abad"
10 add wave -divider "4/7/21"
11 add wave -divider "Project: FIR Filters"
12 add wave -divider "Inputs:"
13 add wave rst clk x
14 add wave -divider "Internal:"
15 #add wave shift_reg
16 add wave sum prod
17 add wave -divider "Outputs:"
18 add wave y
19
20 ##### Add stimuli data
21 force rst 0 0ns, 1 10ns
22 force clk 1 0ns, 0 10ns -r 20ns
23 force x 0000 0ns, 0001 10ns, 0000 30ns
24
25 ##### Run the simulation
26 #run 300 ns
27 #runtime for Filter 3:
28 run 500 ns
29 wave zoomfull
30 configure wave -gridperiod 100ns
31 configure wave -timelineunits ns
```

10 Appendix 3

VHDL Code for Transpose Form FIR Digital Filter

```

2  LIBRARY ieee;
3  USE ieee.std_logic_1164.ALL;
4  USE ieee.numeric_std.ALL;
5
6  ENTITY fir_direct IS
7  GENERIC (
8      NUM_COEF : NATURAL := 11;
9      BITS_COEF : NATURAL := 4;
10     BITS_IN : NATURAL := 4;
11     BITS_OUT : NATURAL := 10);
12  PORT (
13     clk, rst : IN STD_LOGIC;
14     x : IN STD_LOGIC_VECTOR(BITS_IN-1 DOWNT0 0);
15     y : OUT STD_LOGIC_VECTOR(BITS_OUT-1 DOWNT0 0));
16  END ENTITY;
17
18  ARCHITECTURE fpga OF fir_direct IS
19     TYPE int_array IS ARRAY (0 TO NUM_COEF-1) OF INTEGER RANGE
20         -2**(BITS_COEF-1) TO 2**(BITS_COEF-1)-1;
21     CONSTANT coef : int_array := (-8,-5,-5,-1,1,2,2,3,5,7,7);
22     TYPE signed_array IS ARRAY (natural range <>) OF SIGNED;
23     SIGNAL prod : signed_array(NUM_COEF DOWNT0 1)(BITS_IN+BITS_COEF-1 DOWNT0 0);
24     SIGNAL sum : signed_array(NUM_COEF DOWNT0 1)(BITS_OUT-1 DOWNT0 0);
25  BEGIN
26     PROCESS(clk,rst)
27     BEGIN
28         IF rst = '0' THEN
29             sum <= (OTHERS => (OTHERS => '0'));
30         ELSIF rising_edge(clk) THEN
31             sum(NUM_COEF) <= resize(prod(NUM_COEF),BITS_OUT);
32             adder: FOR i IN NUM_COEF-1 DOWNT0 1 LOOP
33                 sum(i) <= sum(i+1) + prod(i);
34             END LOOP;
35             --insert mult, y here for pipeline
36         END IF;
37     END PROCESS;
38
39     mult: FOR i IN NUM_COEF DOWNT0 1 GENERATE
40         prod(i) <= TO_SIGNED(coef(i-1),BITS_COEF) * SIGNED(x);
41     END GENERATE;
42
43     y <= STD_LOGIC_VECTOR(sum(1));
44  END ARCHITECTURE;

```

11 Appendix 4

VHDL Code for Transpose Form FIR Digital Filter (Pipelined Ver.)

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.numeric_std.ALL;
4
5  ENTITY fir_direct IS
6  GENERIC (
7      NUM_COEF : NATURAL := 11;
8      BITS_COEF : NATURAL := 4;
9      BITS_IN : NATURAL := 4;
10     BITS_OUT : NATURAL := 10);
11  PORT (
12     clk, rst : IN STD_LOGIC;
13     x : IN STD_LOGIC_VECTOR(BITS_IN-1 DOWNTO 0);
14     y : OUT STD_LOGIC_VECTOR(BITS_OUT-1 DOWNTO 0));
15  END ENTITY;
16
17  ARCHITECTURE fpga OF fir_direct IS
18     TYPE int_array IS ARRAY (0 TO NUM_COEF-1) OF INTEGER RANGE
19         -2**(BITS_COEF-1) TO 2**(BITS_COEF-1)-1;
20     CONSTANT coef : int_array := (-8,-5,-5,-1,1,2,2,3,5,7,7);
21     TYPE signed_array IS ARRAY (natural range <>) OF SIGNED;
22     SIGNAL prod : signed_array(NUM_COEF DOWNTO 1)(BITS_IN+BITS_COEF-1 DOWNTO 0);
23     SIGNAL sum : signed_array(NUM_COEF DOWNTO 1)(BITS_OUT-1 DOWNTO 0);
24  BEGIN
25     PROCESS(clk,rst)
26     BEGIN
27         IF rst = '0' THEN
28             sum <= (OTHERS => (OTHERS => '0'));
29             prod <= (OTHERS => (OTHERS => '0'));
30             y <= (OTHERS => '0');
31         ELSIF rising_edge(clk) THEN
32             sum(NUM_COEF) <= resize(prod(NUM_COEF),BITS_OUT);
33             adder: FOR i IN NUM_COEF-1 DOWNTO 2 LOOP --changed loop range to eliminate unnecessary resistor
34                 sum(i) <= sum(i+1) + prod(i);
35             END LOOP;
36             --insert mult, y here for pipeline
37             mult: FOR i IN NUM_COEF DOWNTO 1 LOOP
38                 prod(i) <= TO_SIGNED(coef(i-1),BITS_COEF) * SIGNED(x);
39             END LOOP;
40             --calculate output manually
41             y <= STD_LOGIC_VECTOR(sum(2) + prod(1));
42         END IF;
43     END PROCESS;
44  END ARCHITECTURE;

```

12 Appendix 5

VHDL Code for Transposed Form FIR Digital Filter (Pipelined Ver.)

- Used for Step 6 Low Pass Filter Implementation

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.numeric_std.ALL;
4
5  ENTITY fir_direct IS
6  GENERIC (
7      NUM_COEF : NATURAL := 21;
8      BITS_COEF : NATURAL := 10;
9      BITS_IN : NATURAL := 4;
10     BITS_OUT : NATURAL := 16);
11  PORT (
12     clk, rst : IN STD_LOGIC;
13     x : IN STD_LOGIC_VECTOR(BITS_IN-1 DOWNTO 0);
14     y : OUT STD_LOGIC_VECTOR(BITS_OUT-1 DOWNTO 0));
15  END ENTITY;
16
17  ARCHITECTURE fpga OF fir_direct IS
18     TYPE int_array IS ARRAY (0 TO NUM_COEF-1) OF INTEGER RANGE
19         -2**(BITS_COEF-1) TO 2**(BITS_COEF-1)-1;
20     CONSTANT coef : int_array := (-10,-18,-6,28,44,2,-64,-52,100,311,410,311,100,-52,-64,2,44,28,-6,-18,-10);
21     TYPE signed_array IS ARRAY (natural range <>) OF SIGNED;
22     SIGNAL prod : signed_array(NUM_COEF DOWNTO 1)(BITS_IN+BITS_COEF-1 DOWNTO 0);
23     SIGNAL sum : signed_array(NUM_COEF DOWNTO 1)(BITS_OUT-1 DOWNTO 0);
24  BEGIN
25     PROCESS(clk,rst)
26     BEGIN
27         IF rst = '0' THEN
28             sum <= (OTHERS => (OTHERS => '0'));
29             prod <= (OTHERS => (OTHERS => '0'));
30             y <= (OTHERS => '0');
31         ELSIF rising_edge(clk) THEN
32             sum(NUM_COEF) <= resize(prod(NUM_COEF),BITS_OUT);
33             adder: FOR i IN NUM_COEF-1 DOWNTO 2 LOOP
34                 sum(i) <= sum(i+1) + prod(i);
35             END LOOP;
36             mult: FOR i IN NUM_COEF DOWNTO 1 LOOP
37                 prod(i) <= TO_SIGNED(coef(i-1),BITS_COEF) * SIGNED(x);
38             END LOOP;
39             y <= STD_LOGIC_VECTOR(sum(2) + prod(1));
40         END IF;
41     END PROCESS;
42  END ARCHITECTURE;
```

END OF DOCUMENT